ELECTRONICS HUB

PROJECTS | TUTORIALS | COURSES | KITS

CONTACT US

YOU ARE HERE: HOME / DIY PROJECTS / DIY SOLAR BATTERY CHARGER FOR 18650 LI-ION BATTERIES

DIY Solar Battery Charger for 18650 Lilon Batteries

MAY 22, 2019 BY RAVI — LEAVE A COMMENT



In this DIY project, I will show you how to design and build a simple but effective Solar Battery Charger for 18650 batteries. Using this project, you can charge two 18650 Li-Ion batteries directly from solar without any wall adapter.



Table of Contents



- 1. Introduction
- 2. Circuit Diagram
- 3. Components Required
- 4. How to Setup DIY Solar Battery Charger for 18650?
- 5. Principle of DIY Solar Battery Charger for 18650

Introduction

The need for sustainable living has led to the increased usage of renewable energy. Keeping aside the efficiency numbers, Solar Energy is one of the convenient alternatives (when compared to other renewable energy sources such as wind) to the grid supply.

Now-a-days, large Solar Farms are being setup in acres of barren lands in many countries. But small-scale solar plants like on independent building rooftops and near small home communities are also becoming popular.


The setup of a Solar Power Plant. whether large or small, is fairly simple. Setup an array of Solar Panels on rooftop, connect them to a Solar Charge Controller and charge the batteries. From the batteries, you can run any mains appliances using appropriate inverters.

As a beginner's solar project, I have designed a very simple Solar Battery Charger to charge 18650 Li-Ion batteries. Using these batteries, you can charge your mobile phones, tablets or use the batteries in LED Lamps, emergency lights etc.



Circuit Diagram

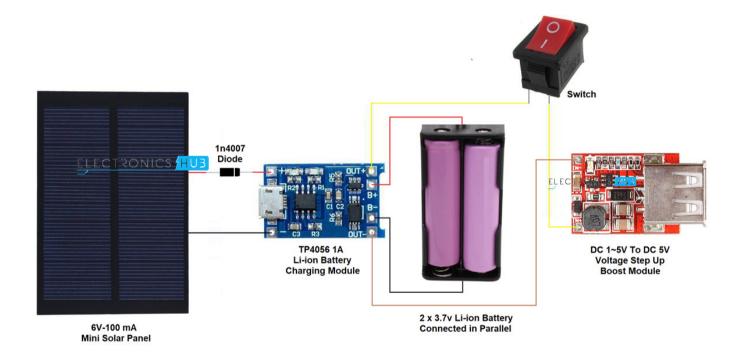Let us dive into the project by taking a look at the circuit diagram or rather the connection diagram of this DIY Solar Battery Charger for 18650. All the components, which I will list out in the next section, are very easy to acquire and are easily available in local electronics stores (you can get them online as well).



Components Required

- 6V 100mA Mini Solar Panel
- 2 x 18650 Li-lon Batteries
- 18650 Battery Holders
- TP4056 Li-Ion Battery Charger Module with protection



- 1V to 5V Input to 5V Output Step-up Converter (Boost Converter)
- 1N4007 PN Junction Diode
- Switch (Push to ON and Push to OFF)
- Connecting Wires
- "For more information on TP4056 Li-Ion Battery Charger Module, read "TP4056 Lithium Ion Battery Charger".


How to Setup DIY Solar Battery Charger for 18650?

First, I will explain the connections and the step by step setup of the Solar Battery Charger for 18650. Then we will understand the principle of operation.

Coming to the connections, the Mini Solar Panel has two wires coming from it. One is Red, which is the positive wire and the other is black (or brown in my case), which is the negative wire.



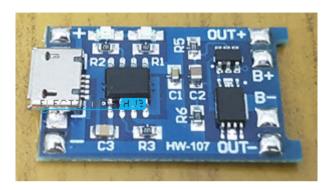
Now, take the TP4056 Li-Ion Battery Charger Module with battery protection. At the input side, it has two connections named IN+ and IN-. Take the Red wire from the solar panel and connect it to the anode of 1N4007 Diode.



Connect the cathode of the diode to the IN+ terminal of the TP4056 Module and directly connect the black wire of the solar panel to the IN- terminal of TP4056. This completes the input section.

On the output side of the TP4056, there are four connections named B+, B-, OUT+ and OUT-. Take two 18650 Li-lon batteries with holders and connect them in parallel i.e. both positive terminals of the batteries are common and both negative terminals are common.

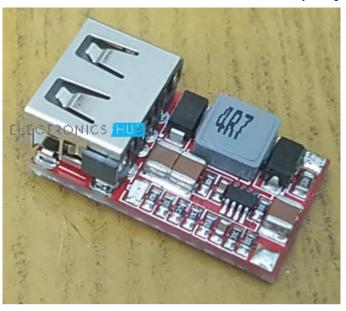Connect the common positive terminal of the batteries to B+ of TP4056. You may have to solder the wires on to the Li-Ion Charger board. Similarly, connect the common negative terminal of the batteries to the B- of TP4056.



The final step of the constriction is to connect the output of the TP4056 to the 5V Boost Converter Module. The Step-up converter module has two input terminals named IN+ and IN-. Connect the OUT+ of TP4056 to IN+ of Boost Converter module and OUT- to IN- respectively.

You can use a switch between TP4056 and Boost converter so that you can turn ON or OFF the output. I have glued the entire setup on to the battery holder case with a switch in the center and the USB port on the edge.




Principle of DIY Solar Battery Charger for 18650

The solar panel used in this project is small 6V panel with a small output of 100mA. The output of this solar panel will not be a constant 6V but it might fluctuate between 5V and 7.5V (as per its data sheet).

This voltage is given as input to the TP4056 Li-Ion Battery Charging Module, which in this scenario, acts as a Solar Charge Controller. The input to TP4056 can be in the range of 4V to 8V (which is the range of the output of the solar panel).

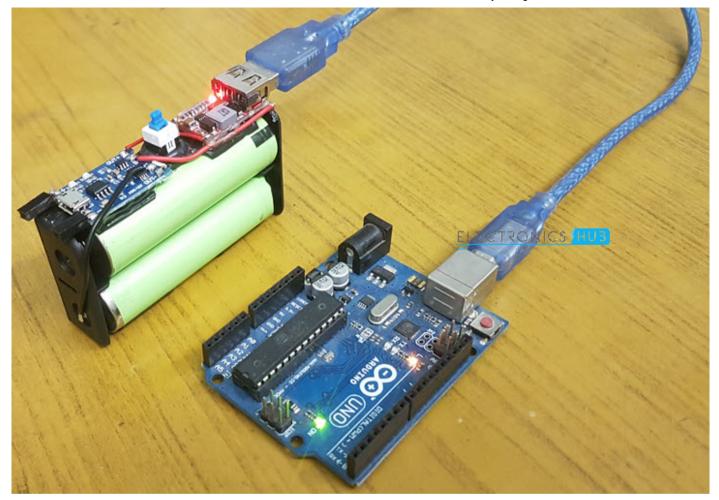TP4056 then charges the battery from the solar power itself. If you only want to charge the batteries, then this is sufficient. But since our project also needs to charge a Mobile Phone, we need to have a 5V output and the output of the 18650 Li-lon batteries is only 3.7V.





Here comes the Boost Converter to the rescue. The boost converter I have used is a 1V-5V input to 5V output step-up converter i.e. it takes an input anywhere between 1V and 5V and produces a constant 5V output. Also, this boost converter can support a current up to 1A, so the charging of mobile phone will not be that slow.

I have used the project to charge my mobile phone as well as to power up an Arduino board.





Email *			
Website			
POST COM	IMENT		

Search this website

PCB Assembly Services



PROJECTS BY CATEGORY

Arduino Projects (200+)

Electronics Projects (250+)

Mini Project Circuits (160+)

Mini Project Ideas (150+)

ECE Projects (150+)

EEE Projects (150+)

8051 Projects (110+)

Raspberry Pi Projects (101+)

Electrical Project Ideas (100+)

Embedded Projects (100+)

Latest Electronics Ideas (100+)

Microcontroller Mini Projects (100+)

Robotics Projects (100+)

VLSI Projects (100+)

Solar Projects (100+)

IOT Projects (100+)

Communication Projects (70+)

LED Projects (70+)

Power Electronics Projects (60+)

RFID Projects (60+)

Home Automation Projects (50+)



Matlab Projects (50+)

EIE Projects (50+)

Wireless Projects (50+)

LabView Projects (45+)

Zigbee Projects (45+)

GSM Projects (40+)

555 Timer Circuits (40+)

Sensor Projects (40+)

ARM Projects (60+)

DTMF Projects (30+)

PIC Projects (30+)

Electrical Mini Projects (25)

ESP8266 Projects (15)

KITS

Best Drone Kits [12]

3D Printer Kits [12]

Best Robot Vacuum Clears [14]

Best Waveform Generators [12]

RGB LED Strip Light Kits [20]

Best LED Christmas Light Kits [13]



SUBSCRIBE FOR UPDATES

Enter your email addre



SUBSCRIBE

GENERAL	PROJECTS	PROJECTS	TUTORIALS	TUTORIALS
Tutorials	Electrical	Mini projects	Capacitors	Amplifiers
Symbols	Electronics	Microcontroller	Resistors	IO Devices
Courses	Embedded	Arduino	Filters	Thyristors
Calculator	Power	Solar	Diodes	DC Circuits
Contact	Robotics	Free circuits	Transistors	Number System
HomeZene	ARM	Home Automation		TS EAMCET 2019
	IOT	Seminar Topics		
		Electronics Questions		FOLLOW US
				Instagram
				Youtube
				Facebook
				Google Plus
				Twitter
				A Duit to a co

Copyright © 2019 Electronicshub.org

